

Terminál pro odemčení / zamčení dveří pomocí 4místného PIN kódu

Členové týmu

Adam Hora, Daniel Haluška, Marek Halaš, Jan Honkyš

<https://github.com/janhonkys/Digital-electronics-1/tree/main/Labs/project>

Cíle projektu

Cílem projektu je vytvořit terminál pro odemčení / zamčení dveří pomocí 4místného PIN kódu, s použitím 4x3 tlačítek, 4 sedmisegmentových displejů, relé pro ovládání zámku dveří.

Návrh vizualizace řešení

 Screenshot

Stavový diagram process p_result controller

 Screenshot

Stavový diagram process p_keypad watcher

 Screenshot

Popis hardwaru

Základní deska Arty A7-100T

Parametry: 4 přepínače, 4 tlačítka, 1 tlačítko reset, 4 LEDs, 4 RGB LEDs, interní hodinový signál, 4 PMOD rozhraní, USB-UART rozhraní

 Screenshot

Klávesnice

Klávesnice je vzhledem k počtu vstupů na základní desce navržena maticově, 4 řádky, 3 sloupce.

Schéma zapojení klávesnice

 Screenshot

Plošný spoj klávesnice


 Screenshot

 Osazovací plán plošného spoje klávesnice

 


Schéma zapojení displeje

Z důvodu omezených možností základní desky jsme navrhli použití 4 7mi segmentových displejů K121, zapojených se společnou katodou. V obrázku na horní straně schéma zapojení zámku a externí sirény.



Plošný spoj displeje



Osazovací plán plošného spoje displeje



Popis VHDL modulů a simulací

Klávesnice

Klávesnice je navržena tak, že po stisknutí tlačítka se nestane nic, dokud se tlačítko nepustí. Po puštění tlačítka je hodnota zapsaná na 1 impuls hodinového signálu do paměti. Při stlačení několika kláves naráz se nic nestane, při jejich puštění se do paměti zapíše nedefinovaná hodnota.

Převodní tabulka vstupů na výstup

Tlačítko	Výstup	hor_1	hor_2	hor_3	hor_4	ver_1	ver_2	ver_3
0	0000	0	0	0	1	0	1	0
1	0001	1	0	1	0	1	0	0
2	0010	0	0	1	0	0	1	0
3	0011	0	0	1	0	0	0	1
4	0100	0	1	0	0	1	0	0
5	0101	0	1	0	0	0	1	0
6	0110	0	1	0	0	0	0	1
7	0111	1	0	0	0	1	0	0
8	1000	1	0	0	0	0	1	0
9	1001	1	0	0	0	0	0	1
enter	1010	0	0	0	1	1	0	0
cancel	1011	0	0	0	1	0	0	1

Vstupní porty

```

entity keypad_4x3 is
  port(
    clk      : in  std_logic;           -- input for clock
    hor_1     : in  std_logic;           -- input for first row
    hor_2     : in  std_logic;           -- input for second
row
    hor_3     : in  std_logic;           -- input for third row
    hor_4     : in  std_logic;           -- input for fourth
row
    ver_1     : in  std_logic;           -- input for first
column
    ver_2     : in  std_logic;           -- input for second
column
    ver_3     : in  std_logic;           -- input for third
column

    number_o  : out std_logic_vector(4 - 1 downto 0) -- output for number

  );
end keypad_4x3;

```

Architektura

```

architecture Behavioral of keypad_4x3 is

  signal s_number      : std_logic_vector(4 - 1 downto 0);

  constant number_0    : std_logic_vector(4 - 1 downto 0) := b"0000";      --
  setting constants for numbel 0-9 in binary
  constant number_1    : std_logic_vector(4 - 1 downto 0) := b"0001";
  constant number_2    : std_logic_vector(4 - 1 downto 0) := b"0010";
  constant number_3    : std_logic_vector(4 - 1 downto 0) := b"0011";
  constant number_4    : std_logic_vector(4 - 1 downto 0) := b"0100";
  constant number_5    : std_logic_vector(4 - 1 downto 0) := b"0101";
  constant number_6    : std_logic_vector(4 - 1 downto 0) := b"0110";
  constant number_7    : std_logic_vector(4 - 1 downto 0) := b"0111";
  constant number_8    : std_logic_vector(4 - 1 downto 0) := b"1000";
  constant number_9    : std_logic_vector(4 - 1 downto 0) := b"1001";
  constant ENTER       : std_logic_vector(4 - 1 downto 0) := b"1010";      -- for
  enter
  constant CANCEL      : std_logic_vector(4 - 1 downto 0) := b"1011";      -- for
  cancel
  constant UNDEFINED   : std_logic_vector(4 - 1 downto 0) := b"1111";      -- and
  for undefined

begin

  p_output_keypad : process(clk)
    begin

```

```

        if rising_edge(clk) then                                -- defining numbers based
on inputs

        number_o <= UNDEFINED;

        if(hor_1 = '0' AND hor_2 = '0' AND hor_3 = '0' AND hor_4 = '1' AND
ver_1 = '0' AND ver_2 = '1' AND ver_3 = '0')then                -- fourth row and second
column for value 0
            s_number <= number_0;
        elsif(hor_1 = '0' AND hor_2 = '0' AND hor_3 = '1' AND hor_4 = '0' AND
ver_1 = '1' AND ver_2 = '0' AND ver_3 = '0')then                -- third row and first
column for value 1
            s_number <= number_1;
        elsif(hor_1 = '0' AND hor_2 = '0' AND hor_3 = '1' AND hor_4 = '0' AND
ver_1 = '0' AND ver_2 = '1' AND ver_3 = '0')then                -- third row and second
column for value 2
            s_number <= number_2;
        elsif(hor_1 = '0' AND hor_2 = '0' AND hor_3 = '1' AND hor_4 = '0' AND
ver_1 = '0' AND ver_2 = '0' AND ver_3 = '1')then                -- third row and third
column for value 3
            s_number <= number_3;
        elsif(hor_1 = '0' AND hor_2 = '1' AND hor_3 = '0' AND hor_4 = '0' AND
ver_1 = '1' AND ver_2 = '0' AND ver_3 = '0')then                -- second row and first
column for value 4
            s_number <= number_4;
        elsif(hor_1 = '0' AND hor_2 = '1' AND hor_3 = '0' AND hor_4 = '0' AND
ver_1 = '0' AND ver_2 = '1' AND ver_3 = '0')then                -- second row and second
column for value 5
            s_number <= number_5;
        elsif(hor_1 = '0' AND hor_2 = '1' AND hor_3 = '0' AND hor_4 = '0' AND
ver_1 = '0' AND ver_2 = '0' AND ver_3 = '1')then                -- second row and third
column for value 6
            s_number <= number_6;
        elsif(hor_1 = '1' AND hor_2 = '0' AND hor_3 = '0' AND hor_4 = '0' AND
ver_1 = '1' AND ver_2 = '0' AND ver_3 = '0')then                -- first row and first
column for value 7
            s_number <= number_7;
        elsif(hor_1 = '1' AND hor_2 = '0' AND hor_3 = '0' AND hor_4 = '0' AND
ver_1 = '0' AND ver_2 = '1' AND ver_3 = '0')then                -- first row and second
column for value 8
            s_number <= number_8;
        elsif(hor_1 = '1' AND hor_2 = '0' AND hor_3 = '0' AND hor_4 = '0' AND
ver_1 = '0' AND ver_2 = '0' AND ver_3 = '1')then                -- first row and third
column for value 9
            s_number <= number_9;
        elsif(hor_1 = '0' AND hor_2 = '0' AND hor_3 = '0' AND hor_4 = '1' AND
ver_1 = '1' AND ver_2 = '0' AND ver_3 = '0')then                -- fourth row and first
column for ENTER
            s_number <= ENTER;
        elsif(hor_1 = '0' AND hor_2 = '0' AND hor_3 = '0' AND hor_4 = '1' AND
ver_1 = '0' AND ver_2 = '0' AND ver_3 = '1')then                -- fourth row and third
column for CANCEL
            s_number <= CANCEL;

```

```

        elsif(hor_1 = '0' AND hor_2 = '0' AND hor_3 = '0' AND hor_4 = '0' AND
ver_1 = '0' AND ver_2 = '0' AND ver_3 = '0')then      -- if we don't have inputs,
then number is undefined
            number_o <= s_number;      --
            s_number <= UNDEFINED;
        else      -- if have been pressed 2 or more
buttons in same time, then number is undefined
            number_o <= UNDEFINED;
        end if;

        end if; -- Synchronous reset

    end process p_output_keypad;

end Behavioral;
```

Testbench klávesnice

```

architecture Behavioral of tb_keypad_4x3 is

    constant c_CLK_100MHZ_PERIOD : time := 10 ns;
    signal s_clk_100MHz      : std_logic;
    signal s_hor_1 : std_logic;
    signal s_hor_2 : std_logic;
    signal s_hor_3 : std_logic;
    signal s_hor_4 : std_logic;
    signal s_ver_1 : std_logic;
    signal s_ver_2 : std_logic;
    signal s_ver_3 : std_logic;
    signal s_number_i : std_logic_vector(4 - 1 downto 0);

begin
    uut_keypad_4x3 : entity work.keypad_4x3
        port map(
            clk      => s_clk_100MHz,
            hor_1    => s_hor_1,
            hor_2    => s_hor_2,
            hor_3    => s_hor_3,
            hor_4    => s_hor_4,
            ver_1    => s_ver_1,
            ver_2    => s_ver_2,
            ver_3    => s_ver_3,
            number_o => s_number_i
        );

    p_clk_gen : process
    begin
        while now < 100000000 ns loop      -- 10 usec of simulation
            s_clk_100MHz <= '0';
            wait for c_CLK_100MHZ_PERIOD / 2;
```

```

        s_clk_100MHz <= '1';
        wait for c_CLK_100MHZ_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;

p_stimulus : process
begin

    s_hor_1 <= '0';
    s_hor_2 <= '0';
    s_hor_3 <= '0';
    s_hor_4 <= '0';
    s_ver_1 <= '0';
    s_ver_2 <= '0';
    s_ver_3 <= '0';

    s_hor_4 <= '1';           --0
    s_ver_2 <= '1';
    wait for 40 ns;
    s_hor_4 <= '0';           --0
    s_ver_2 <= '0';
    wait for 40 ns;

    s_hor_1 <= '1';           --1
    s_hor_3 <= '1';
    s_ver_1 <= '1';
    wait for 40 ns;
    s_hor_1 <= '0';           --1
    s_hor_3 <= '0';
    s_ver_1 <= '0';
    wait for 40 ns;

    s_hor_3 <= '1';           --2
    s_ver_2 <= '1';
    wait for 40 ns;
    s_hor_3 <= '0';           --2
    s_ver_2 <= '0';
    wait for 40 ns;

    s_hor_3 <= '1';           --3
    s_ver_3 <= '1';
    wait for 40 ns;
    s_hor_3 <= '0';           --3
    s_ver_3 <= '0';
    wait for 40 ns;

    s_hor_2 <= '1';           --4
    s_ver_1 <= '1';
    wait for 40 ns;
    s_hor_2 <= '0';
    s_ver_1 <= '0';
    wait for 40 ns;

```

```
s_hor_2 <= '1';      --5
s_ver_2 <= '1';
wait for 40 ns;
s_hor_2 <= '0';
s_ver_2 <= '0';
wait for 40 ns;

s_hor_2 <= '1';      --6
s_ver_3 <= '1';
wait for 40 ns;
s_hor_2 <= '0';
s_ver_3 <= '0';
wait for 40 ns;

s_hor_1 <= '1';      --7
s_ver_1 <= '1';
wait for 40 ns;
s_hor_1 <= '0';
s_ver_1 <= '0';
wait for 40 ns;

s_hor_1 <= '1';      --8
s_ver_2 <= '1';
wait for 40 ns;
s_hor_1 <= '0';
s_ver_2 <= '0';
wait for 40 ns;

s_hor_1 <= '1';      --9
s_ver_3 <= '1';
wait for 40 ns;
s_hor_1 <= '0';
s_ver_3 <= '0';
wait for 40 ns;

s_hor_4 <= '1';      --enter
s_ver_1 <= '1';
wait for 40 ns;
s_hor_4 <= '0';
s_ver_1 <= '0';
wait for 40 ns;

s_hor_4 <= '1';      --cancel
s_ver_3 <= '1';
wait for 40 ns;
s_hor_4 <= '0';
s_ver_3 <= '0';
wait for 40 ns;

wait;
wait;
end process p_stimulus;
```

```
end Behavioral;
```

Screenshot simulace tb_keypad

Postupně zkusíme stisknutí jednotlivých tlačítek, simulace proběhla v pořádku, výstupní signál odpovídá převodní tabulce.



Hlavní řídicí jednotka

Slouží ke zpracování vstupního signálu z klávesnice, který se podle rozhodovacího kritéria posoudí, jestli odpovídá správnému heslu. Když odpovídá správnému heslu, které je nastaveno na kombinaci čísel 2222, zámek dveří se otevře. Po dobu 10s budou dveře otevřeny (v simulaci nastaveno 1000ns), poté se zámek dveří zavře a čeká se na zavření dveří 10s (v simulaci 1000 ns), pokud se dveře do časového intervalu nezavřou (signál door_i), spustí se alarm, který je možný resetovat master heslem 1111. Při otevření dveří použitím master hesla je zámek otevřený na 10s (v simulaci 1000ns), ale následně se nečeká na zavření dveří, nespustí se alarm. Vstupní signál z klávesnice je zpracován na výstupní signály, které jsou předány ovladači 4 7mi segmentových displejů.

Vstupní porty

```
entity controler is
  port(
    clk      : in  std_logic;           -- input for
    clock
    reset    : in  std_logic;           -- input for
    reset
    number_i : in  std_logic_vector(4 - 1 downto 0); -- input for
    number
    door_i    : in  std_logic;           -- input for
    door
    alarm_o   : out std_logic;           -- output for
    alarm
    locker_o  : out std_logic;           -- output for
    "locker"

    rgb_o     : out std_logic_vector(3 - 1 downto 0); -- output for
    RGB diode

    data0_o   : out std_logic_vector(4 - 1 downto 0); -- output for
    first number of password
    data1_o   : out std_logic_vector(4 - 1 downto 0); -- output for
    second number of password
    data2_o   : out std_logic_vector(4 - 1 downto 0); -- output for
    third number of password
    data3_o   : out std_logic_vector(4 - 1 downto 0); -- output for
    fourth number of password
```



```
);
end controler;
```

Architektura

```
architecture Behavioral of controler is

    type t_state is (CLOSE, OPENED, WAITH, AFTERTIME, ALARM, MASTER);
-- types of states
    signal s_state : t_state;
-- assign state to signal

    type t_state_pass is (POS1, POS2, POS3, POS4, ENT);
-- types of states by pressing of buttons
    signal s_state_pass : t_state_pass;
-- assign state_pass to signal

    signal s_clk : std_logic;
-- signal for clock

    signal s_cnt : unsigned(32 - 1 downto 0) :=
b"0000_0000_0000_0000_0000_0000_0000_0000"; -- nejak neviem zisti? ?o je to s_cnt

    signal s_alarm : std_logic; -- signal for
alarm
    signal s_reset_pass : std_logic; -- signal for
reset password

    signal s_pass_1 : std_logic_vector(4 - 1 downto 0); -- signal for
first password position
    signal s_pass_2 : std_logic_vector(4 - 1 downto 0); -- for second
    signal s_pass_3 : std_logic_vector(4 - 1 downto 0); -- for third
    signal s_pass_4 : std_logic_vector(4 - 1 downto 0); -- for last
    signal s_pass : std_logic_vector(16 - 1 downto 0); -- signal for
whole password

    constant c_DELAY_10SEC : unsigned(32 - 1 downto 0) :=
b"0000_0000_0000_0000_0000_0000_0110_0100"; -- time constant for 10s (but
changed to 100ns, becose we want see that in our simulation)
    constant c_ZERO : unsigned(32 - 1 downto 0) :=
b"0000_0000_0000_0000_0000_0000_0000_0000"; -- time constant for 0s

    constant c_MASTER_pass : std_logic_vector(16 - 1 downto 0) :=
b"0001_0001_0001_0001"; -- master password is 1111
    constant c_SLAVE_pass : std_logic_vector(16 - 1 downto 0) :=
b"0010_0010_0010_0010"; -- normal password is 2222
    constant c_UNDEFINED_pass : std_logic_vector(16 - 1 downto 0) :=
b"1111_1111_1111_1111"; -- undefined password
```

```

    constant c_UNDEFINED : std_logic_vector(4 - 1 downto 0) := b"1111";
-- constant for unexistent button
    constant c_CANCEL : std_logic_vector(4 - 1 downto 0) := b"1011";
-- constant for cancel
    constant c_ENTER : std_logic_vector(4 - 1 downto 0) := b"1010";
-- constant for enter

    constant c_RED : std_logic_vector(3 - 1 downto 0) := b"100";
-- constants for rgb diode    - for red
    constant c_GREEN : std_logic_vector(3 - 1 downto 0) := b"010";
--                            - for green
    constant c_YELLOW : std_logic_vector(3 - 1 downto 0) := b"110";
--                            - for yellow

begin

p_keypad_watcher : process(clk, s_reset_pass, reset)
begin

    if reset = '1' then
        s_pass <= c_UNDEFINED_pass;                -- password will be
undefined
        s_pass_1 <= c_UNDEFINED;                    -- first position will
be undefined
        s_pass_2 <= c_UNDEFINED;                    -- second
        s_pass_3 <= c_UNDEFINED;                    -- third
        s_pass_4 <= c_UNDEFINED;
        s_state_pass <= POS1;

    else
        if s_reset_pass = '1' then -- treba dako vyhutat        -- if s_reset_pass
= 1 then
            s_pass <= c_UNDEFINED_pass;                -- password will
be undefined
            s_pass_1 <= c_UNDEFINED;                    -- first position
will be undefined
            s_pass_2 <= c_UNDEFINED;                    -- second
            s_pass_3 <= c_UNDEFINED;                    -- third
            s_pass_4 <= c_UNDEFINED;                    -- and last
        end if;

        if falling_edge(clk) then

            if(number_i = c_UNDEFINED)then

                                                                -- proces for
enter password
            else

                case (s_state_pass) is
                    when POS1 =>

-- assign first position
                        if (number_i = c_CANCEL OR number_i = c_ENTER)then

```

```
-- if is pressed cancel or enter
                                s_pass_1 <= c_UNDEFINED;
-- then first position will be undefined
                                s_pass_2 <= c_UNDEFINED;
-- second
                                s_pass_3 <= c_UNDEFINED;
-- third
                                s_pass_4 <= c_UNDEFINED;
-- fourth
                                s_state_pass <= POS1;
-- and whole password
                                else
                                    s_pass_1 <= number_i;
-- if it is number 1-9 then we have first position
                                    s_state_pass <= POS2;
-- and change state to POS2
                                end if;

                                when POS2 =>

-- pos2
                                if (number_i = c_CANCEL OR number_i = c_ENTER)then
-- same as pos1
                                    s_pass_1 <= c_UNDEFINED;
                                    s_pass_2 <= c_UNDEFINED;
                                    s_pass_3 <= c_UNDEFINED;
                                    s_pass_4 <= c_UNDEFINED;
                                    s_state_pass <= POS1;
                                else
                                    s_pass_2 <= number_i;
-- now we have second position
                                    s_state_pass <= POS3;
-- and change state to POS3
                                end if;

                                when POS3 =>

-- same as pos2
                                if (number_i = c_CANCEL OR number_i = c_ENTER)then
                                    s_pass_1 <= c_UNDEFINED;
                                    s_pass_2 <= c_UNDEFINED;
                                    s_pass_3 <= c_UNDEFINED;
                                    s_pass_4 <= c_UNDEFINED;
                                    s_state_pass <= POS1;
                                else
                                    s_pass_3 <= number_i;
                                    s_state_pass <= POS4;
                                end if;

                                when POS4 =>

-- same as pos2
                                if (number_i = c_CANCEL)then
                                    s_pass_1 <= c_UNDEFINED;
                                    s_pass_2 <= c_UNDEFINED;
                                    s_pass_3 <= c_UNDEFINED;
```

```

        s_pass_4 <= c_UNDEFINED;
        s_state_pass <= POS1;
    else
        s_pass_4 <= number_i;
        s_state_pass <= ENT;
-- but state will be changed to ENT
    end if;

    when ENT =>
-- state ENT
        if (number_i = c_CANCEL) then
-- if is pressed CANCEL
            s_pass_1 <= c_UNDEFINED;
-- then first position will be undefined
            s_pass_2 <= c_UNDEFINED;
-- second
            s_pass_3 <= c_UNDEFINED;
-- third
            s_pass_4 <= c_UNDEFINED;
-- forth
            s_state_pass <= POS1;
-- and whole password
        elsif (number_i = c_ENTER) then
-- if is pressed ENTER
            s_state_pass <= POS1;
-- state will change to POS1
            s_pass <= s_pass_1 & s_pass_2 & s_pass_3 &
s_pass_4 ; -- pass_1, pass_2, pass_3 nad pass_4 will be merged
            s_pass_1 <= c_UNDEFINED; -- abo nejaky znak iny
-- then all password position will be undefined
            s_pass_2 <= c_UNDEFINED;
            s_pass_3 <= c_UNDEFINED;
            s_pass_4 <= c_UNDEFINED;
        else
            s_state_pass <= ENT;
-- if we dont press enter or cancel then we are again in ENT
        end if;
        when others =>
            s_state_pass <= POS1;
-- else state is again pos1
        end case;

    end if;

end if;
end process p_keypad_watcher;

p_result_controler : process(clk, reset)
proces for result
begin

    if reset = '1' then

```

```

    s_state <= CLOSE;
    locker_o <= '0';
    rgb_o <= c_RED;
    s_alarm <= '0';

else

    if rising_edge(clk) then

        case s_state is

            when CLOSE =>
-- state close

                if ((s_pass = c_MASTER_pass) OR (s_pass =
c_SLAVE_pass))then
                    -- if password is righth (1111 or 2222)
                    s_state <= OPENED; -- mozna led
-- then state is changed to opened
                else
                    s_state <= CLOSE; -- mozna led
-- else
                    locker_o <= '0';
-- door is locked
                    rgb_o <= c_RED;
-- and color of diode is red
                end if;

            when OPENED =>
state opened
--

                if (s_cnt < c_DELAY_10SEC) then
the time is less than 10s
-- if

                    s_cnt <= s_cnt + 1;
                    locker_o <= '1';
then door will be opened
--

                    rgb_o <= c_GREEN;
diode is green
-- and

                else
                    s_state <= WAITH;
is time more than 10s
-- if

                    locker_o <= '0';
door will be closed
--

                    s_cnt <= c_ZERO;
time is reset (0)
-- and

                end if;

            when WAITH =>
state waith
--

                if (s_cnt < c_DELAY_10SEC) then
the time is less than 10s
-- if

                    s_cnt <= s_cnt + 1;
                    rgb_o <= c_YELLOW;
then color of diode will be yellow
--

```

```

        elsif (door_i = '1') then                                -- if
the door will be closed
            s_state <= CLOSE;                                    --
then we go to state close
            s_reset_pass <= '1';                                --
password is reseted
            s_cnt    <= c_ZERO;                                  -- and
time will be reset too
        else
            s_state <= AFTERTIME;                                -- it
the time is more than 10s then we go to state AFTERTIME
            s_cnt    <= c_ZERO;                                  --
time is 0

        end if;

        when AFTERTIME =>                                        --
state aftertime
            if (s_pass = c_MASTER_pass) then                    -- if
was password 1111 (master password)
                s_state <= MASTER;                                --
then state is changed to MASTER
                s_reset_pass <= '1';                            -- and
password is reseted
            else
                s_reset_pass <= '1';                                --
else password is reseted
                s_state <= ALARM;                                  -- and
state is changed to ALARM
            end if;

        when ALARM =>                                           --
state alarm
            s_alarm <= '1';                                        -- if
the alarm is on
            s_state <= CLOSE;                                    --
then we go to state CLOSE

        when MASTER =>                                          --
state master
            if (door_i = '1') then                                -- if
door is closed
                s_state <= CLOSE;                                --
then we go to state CLOSE
            else
                s_state <= MASTER;                                -- if
the door is open
                rgb_o <= c_GREEN;                                  --
then we stay in state MASTER and diode is green
            end if;
        when others =>
            s_state <= CLOSE;                                    --
ielse state is close

```

```

        end case;
    end if;

    if falling_edge(clk) then

        s_reset_pass <= '0';

        if (s_alarm = '1') then -- alarm is on
            if (s_pass = c_MASTER_pass) then -- if the password was
master password
                s_alarm <= '0'; -- then alarm is off
                s_reset_pass <= '1'; -- and password is
reseted

                s_state <= CLOSE;
            else
                s_alarm <= '1'; -- else alarm is on
            end if;
        end if; -- Alarm
    end if; -- Falling edge
end if;
end process p_result_controler;

alarm_o <= s_alarm ; -- signal shift from architecture to
entity (alarm)

data0_o <= s_pass_1; -- signal shift from architecture to
entity (all parts of password)
data1_o <= s_pass_2;
data2_o <= s_pass_3;
data3_o <= s_pass_4;

end Behavioral;
```

Testbench hlavní řídicí jednotky

```

architecture testbench of tb_controler is

    constant c_CLK_100MHZ_PERIOD : time := 10 ns;

    --Local signals
    signal s_clk_100MHz      : std_logic;
    signal s_reset           : std_logic;
    signal s_number_i       : std_logic_vector(4 - 1 downto 0);
    signal s_door_i         : std_logic;
    signal s_alarm_o        : std_logic;
    signal s_locker_o       : std_logic;

    signal s_hor_1 : std_logic;
    signal s_hor_2 : std_logic;
    signal s_hor_3 : std_logic;
    signal s_hor_4 : std_logic;
```

```

signal s_ver_1 : std_logic;
signal s_ver_2 : std_logic;
signal s_ver_3 : std_logic;

signal s_data0_o : std_logic_vector(4-1 downto 0);
signal s_data1_o : std_logic_vector(4-1 downto 0);
signal s_data2_o : std_logic_vector(4-1 downto 0);
signal s_data3_o : std_logic_vector(4-1 downto 0);

signal s_rgb_o : std_logic_vector(3-1 downto 0);

begin
    -- signals shift from controller to signals in this tb
    uut_controller : entity work.controller
        port map(
            clk      => s_clk_100MHz,
            reset    => s_reset,
            number_i => s_number_i,
            door_i   => s_door_i ,
            alarm_o  => s_alarm_o ,
            locker_o => s_locker_o,

            rgb_o => s_rgb_o,

            data0_o => s_data0_o,
            data1_o => s_data1_o,
            data2_o => s_data2_o,
            data3_o => s_data3_o

        );
    -- -- signals shift from keypad to signals in this tb
    uut_keypad_4x3 : entity work.keypad_4x3
        port map(
            clk      => s_clk_100MHz,
            hor_1    => s_hor_1,
            hor_2    => s_hor_2,
            hor_3    => s_hor_3,
            hor_4    => s_hor_4,
            ver_1    => s_ver_1,
            ver_2    => s_ver_2,
            ver_3    => s_ver_3,
            number_o => s_number_i
        );
    -- proces for clock
    p_clk_gen : process
    begin
        while now < 100000000 ns loop
            s_clk_100MHz <= '0';
            wait for c_CLK_100MHZ_PERIOD / 2;
            s_clk_100MHz <= '1';
            wait for c_CLK_100MHZ_PERIOD / 2;
        end while;
    end process;
    -- while is time less than 10s
    -- then clk_100MHz is 0
    -- after 5 ns is 1
    -- and loop until time will be 10s

```



```
        end loop;
        wait;
    end process p_clk_gen;

    p_stimulus : process
    begin

        s_hor_1 <= '0';
        s_hor_2 <= '0';           -- set to 0
        s_hor_3 <= '0';
        s_hor_4 <= '0';
        s_ver_1 <= '0';
        s_ver_2 <= '0';
        s_ver_3 <= '0';
        s_door_i <= '0';

        s_reset <= '1';           -- set reset to 1
        wait for 100 ns;
        s_reset <= '0';           -- set reset to 0
        wait for 10 ns;

        s_hor_3 <= '1';           -- press 1
        s_ver_1 <= '1';
        wait for 40 ns;
        s_hor_3 <= '0';           -- set signals to zero
        s_ver_1 <= '0';
        wait for 40 ns;

        s_hor_3 <= '1';           -- press 1
        s_ver_1 <= '1';
        wait for 40 ns;
        s_hor_3 <= '0';           -- set signals to zero
        s_ver_1 <= '0';
        wait for 40 ns;

        s_hor_4 <= '1';
        s_ver_3 <= '1';           -- press cancel
        wait for 40 ns;
        s_hor_4 <= '0';           -- set signal to zero
        s_ver_3 <= '0';
        wait for 40 ns;

        s_hor_3 <= '1';           -- press 2
        s_ver_2 <= '1';
        wait for 40 ns;
        s_hor_3 <= '0';           -- set signals to zero
        s_ver_2 <= '0';
        wait for 40 ns;

        s_hor_3 <= '1';           -- press 2
        s_ver_2 <= '1';
        wait for 40 ns;
```

```
s_hor_3 <= '0';           -- set signals to zero
s_ver_2 <= '0';
wait for 40 ns;

s_hor_3 <= '1';           -- press 2
s_ver_2 <= '1';
wait for 40 ns;
s_hor_3 <= '0';           -- set signals to zero
s_ver_2 <= '0';
wait for 40 ns;

s_hor_3 <= '1';           -- press 2
s_ver_2 <= '1';
wait for 40 ns;
s_hor_3 <= '0';           -- set signals to zero
s_ver_2 <= '0';
wait for 40 ns;

s_hor_4 <= '1';           -- press enter
s_ver_1 <= '1';
wait for 40 ns;
s_hor_4 <= '0';           -- set signals to zero
s_ver_1 <= '0';

wait for 1.6 us;
s_door_i <= '1';          -- door will be closed
wait for 40 ns;

wait for 1 us;

s_hor_3 <= '1';           -- press 2
s_ver_2 <= '1';
wait for 40 ns;
s_hor_3 <= '0';           -- set signals to zero
s_ver_2 <= '0';
wait for 40 ns;

s_hor_3 <= '1';           -- press 2
s_ver_2 <= '1';
wait for 40 ns;
s_hor_3 <= '0';           -- set signals to zero
s_ver_2 <= '0';
wait for 40 ns;

s_hor_3 <= '1';           -- press 2
s_ver_2 <= '1';
wait for 40 ns;
s_hor_3 <= '0';           -- set signals to zero
s_ver_2 <= '0';
wait for 40 ns;

s_hor_3 <= '1';           -- press 2
s_ver_2 <= '1';
```

```
wait for 40 ns;
s_hor_3 <= '0';
s_ver_2 <= '0';
wait for 40 ns;

s_hor_4 <= '1';
s_ver_1 <= '1';
wait for 40 ns;
s_hor_4 <= '0';
s_ver_1 <= '0';
wait for 40 ns;
s_door_i <= '0';
wait for 2 us;

s_hor_3 <= '1';
s_ver_1 <= '1';
wait for 40 ns;
s_hor_3 <= '0';
s_ver_1 <= '0';
wait for 40 ns;

s_hor_3 <= '1';
s_ver_1 <= '1';
wait for 40 ns;
s_hor_3 <= '0';
s_ver_1 <= '0';
wait for 40 ns;

s_hor_3 <= '1';
s_ver_1 <= '1';
wait for 40 ns;
s_hor_3 <= '0';
s_ver_1 <= '0';
wait for 40 ns;

s_hor_3 <= '1';
s_ver_1 <= '1';
wait for 40 ns;
s_hor_3 <= '0';
s_ver_1 <= '0';
wait for 40 ns;

s_hor_4 <= '1';
s_ver_1 <= '1';
wait for 40 ns;
s_hor_4 <= '0';
s_ver_1 <= '0';

wait;

wait;
end process p_stimulus;
end testbench;
```

Screenshot simulace tb_controller

Na začátku zkusíme zadat 2 čísla, poté stlačíme cancel. S_state_pass se vrátil na POS1. Následně zadáme správné heslo, potvrdíme enter, dveře se otevřou na dobu 1000 ns, následně jsou dveře zavřené, nedojde ke spuštění alarmu. Po chvíli zadáme správné heslo, ale dveře nezavřeme, zapne se alarm. Alarm se zruší zadáním master hesla 1111, při tomto zadání nedojde k otevření dveří, toto heslo se používá pro zrušení alarmu.



Ovladač 4 7mi segmentových displejů

Vstupní porty

```
entity driver_7seg_4digits is
  port(
    clk      : in  std_logic;          -- Main clock
    reset    : in  std_logic;          -- Synchronous reset
    -- 4-bit input values for individual digits
    data0_i  : in  std_logic_vector(4 - 1 downto 0);
    data1_i  : in  std_logic_vector(4 - 1 downto 0);
    data2_i  : in  std_logic_vector(4 - 1 downto 0);
    data3_i  : in  std_logic_vector(4 - 1 downto 0);

    -- Cathode values for individual segments
    seg_o    : out std_logic_vector(7 - 1 downto 0);
    -- Common anode signals to individual displays
    dig_o    : out std_logic_vector(4 - 1 downto 0)
  );
end entity driver_7seg_4digits;
```

Architektura

```
architecture Behavioral of driver_7seg_4digits is

  -- Internal clock enable
  signal s_en : std_logic;
  -- Internal 2-bit counter for multiplexing 4 digits
  signal s_cnt : std_logic_vector(2 - 1 downto 0);
  -- Internal 4-bit value for 7-segment decoder
  signal s_hex : std_logic_vector(4 - 1 downto 0);

begin
  -----
  -- Instance (copy) of clock_enable entity generates an enable pulse
  -- every 4 ms
  clk_en0 : entity work.clock_enable
    generic map(
```

```

        --- WRITE YOUR CODE HERE
        g_MAX => 4 --400000

    )
    port map(
        --- WRITE YOUR CODE HERE
        clk =>clk,          -- Main clock
        reset =>reset,      -- Synchronous reset
        ce_o  =>s_en        -- Clock enable pulse signal
    );

-----

-- Instance (copy) of cnt_up_down entity performs a 2-bit down
-- counter
bin_cnt0 : entity work.cnt_up_down
    generic map(
        --- WRITE YOUR CODE HERE
        g_CNT_WIDTH => 2
    )
    port map(
        --- WRITE YOUR CODE HERE
        clk  => clk,          -- Main clock
        reset =>reset,        -- Synchronous reset
        en_i  =>s_en,         -- Enable input
        cnt_up_i => '0',      -- Direction of the counter
        cnt_o=>s_cnt
    );

-----

-- Instance (copy) of hex_7seg entity performs a 7-segment display
-- decoder
hex2seg : entity work.hex_7seg
    port map(
        hex_i => s_hex,
        seg_o => seg_o
    );

-----

-- p_mux:
-- A combinational process that implements a multiplexer for
-- selecting data for a single digit, a decimal point signal, and
-- switches the common anodes of each display.
-----

p_mux : process(s_cnt, data0_i, data1_i, data2_i, data3_i)
begin
    case s_cnt is
        when "11" =>
            s_hex <= data3_i;
            dig_o <= "0111";

        when "10" =>
            --- WRITE YOUR CODE HERE
            s_hex <= data2_i;
            dig_o <= "1011";
    end case;
end process;

```

```

        when "01" =>
            -- WRITE YOUR CODE HERE
            s_hex <= data1_i;
            dig_o <= "1101";

        when others =>
            -- WRITE YOUR CODE HERE
            s_hex <= data0_i;
            dig_o <= "1110";
    end case;
end process p_mux;

end architecture Behavioral;

```

Hodinový signál

Vstupní porty

```

entity clock_enable is
    generic(
        g_MAX : natural := 10      -- Number of clk pulses to generate
                                    -- one enable signal period
    ); -- Note that there IS a semicolon between generic and port
        -- sections
    port(
        clk   : in  std_logic;      -- Main clock
        reset : in  std_logic;      -- Synchronous reset
        ce_o  : out std_logic       -- Clock enable pulse signal
    );
end entity clock_enable;

```

Architektura

```

architecture Behavioral of clock_enable is

    -- Local counter
    signal s_cnt_local : natural;

begin
    -----
    -- p_clk_ena:
    -- Generate clock enable signal. By default, enable signal is low
    -- and generated pulse is always one clock long.
    -----
    p_clk_ena : process(clk)
    begin
        if rising_edge(clk) then      -- Synchronous process

```

```

        if (reset = '1') then          -- High active reset
            s_cnt_local <= 0;          -- Clear local counter
            ce_o          <= '0';      -- Set output to low

        -- Test number of clock periods
        elsif (s_cnt_local >= (g_MAX - 1)) then
            s_cnt_local <= 0;          -- Clear local counter
            ce_o          <= '1';      -- Generate clock enable pulse

        else
            s_cnt_local <= s_cnt_local + 1;
            ce_o          <= '0';
        end if;
    end if;
end process p_clk_ena;

end architecture Behavioral;

```

Obousměrný čítač

Vstupní porty

```

entity cnt_up_down is
    generic(
        g_CNT_WIDTH : natural := 4      -- Number of bits for counter
    );
    port(
        clk      : in  std_logic;        -- Main clock
        reset    : in  std_logic;        -- Synchronous reset
        en_i     : in  std_logic;        -- Enable input
        cnt_up_i : in  std_logic;        -- Direction of the counter
        cnt_o    : out std_logic_vector(g_CNT_WIDTH - 1 downto 0)
    );
end entity cnt_up_down;

```

Architektura

```

architecture behavioral of cnt_up_down is

    -- Local counter
    signal s_cnt_local : unsigned(g_CNT_WIDTH - 1 downto 0);

begin
    -----
    -- p_cnt_up_down:
    -- Clocked process with synchronous reset which implements n-bit
    -- up/down counter.

```

```
-----
p_cnt_up_down : process(clk)
begin
    if rising_edge(clk) then

        if (reset = '1') then          -- Synchronous reset
            s_cnt_local <= (others => '0'); -- Clear all bits

        elsif (en_i = '1') then        -- Test if counter is enabled

            -- TEST COUNTER DIRECTION HERE
            if (cnt_up_i = '1') then
                s_cnt_local <= s_cnt_local + 1;
            elsif (cnt_up_i = '0') then
                s_cnt_local <= s_cnt_local - 1;
            end if;
        end if;
    end if;
end process p_cnt_up_down;

-- Output must be retyped from "unsigned" to "std_logic_vector"
cnt_o <= std_logic_vector(s_cnt_local);

end architecture behavioral;
```

Dekodér na 7mi segmentový displej

Slouží k převodu vstupního 4 bitového signálu na výstupní 7mi bitový signál, který se zobrazuje na displeji.

Převodní tabulka dekodéru na 7mi segmentový displej

Hex	Vstup	A	B	C	D	E	F	G
0	0000	0	0	0	0	0	0	1
1	0001	1	0	0	1	1	1	1
2	0010	0	0	1	0	0	1	0
3	0011	0	0	0	0	1	1	0
4	0100	1	0	0	1	1	0	0
5	0101	0	1	0	0	1	0	0
6	0110	0	1	0	0	0	0	0
7	0111	0	0	1	1	1	1	1
8	1000	0	0	0	0	0	0	0
9	1001	0	0	0	0	1	0	0
A	1010	0	0	0	1	0	0	0

Hex	Vstup	A	B	C	D	E	F	G
B	1011	1	1	0	0	0	0	0
C	1100	0	1	1	0	0	0	1
D	1101	1	0	0	0	0	1	0
E	1110	0	1	1	0	0	0	0
F	1111	0	1	1	1	0	0	0

Architektura

```

architecture Behavioral of hex_7seg is
begin

  p_7seg_decoder : process(hex_i)
  begin
    case hex_i is
      when "0000" =>
        seg_o <= "0000001";      -- 0
      when "0001" =>
        seg_o <= "1001111";      -- 1
      when "0010" =>
        seg_o <= "0010010";      -- 2
      when "0011" =>
        seg_o <= "0000110";      -- 3
      when "0100" =>
        seg_o <= "1001100";      -- 4
      when "0101" =>
        seg_o <= "0100100";      -- 5
      when "0110" =>
        seg_o <= "0100000";      -- 6
      when "0111" =>
        seg_o <= "0001111";      -- 7
      when "1000" =>
        seg_o <= "0000000";      -- 8
      when "1001" =>
        seg_o <= "0000100";      -- 9
      when "1010" =>
        seg_o <= "0001000";      -- A
      when "1011" =>
        seg_o <= "1100000";      -- B
      when "1100" =>
        seg_o <= "0110001";      -- C
      when "1101" =>
        seg_o <= "1000010";      -- D
      when "1110" =>
        seg_o <= "0110000";      -- E
      when others =>
        seg_o <= "1111111";      -- NOTHING
    end case;
  end process;
end architecture;

```

```

        end process p_7seg_decoder;

    end architecture Behavioral;

```

TOP modul a simulace

Schéma TOP modulu



Vstupní porty

```

entity top is
    Port (
        CLK100MHZ : in STD_LOGIC;

        btn : in STD_LOGIC_VECTOR (4-1 downto 0);    --reset

        ja : in STD_LOGIC_VECTOR (8-1 downto 0);      -- door input for keypad
        jb : out STD_LOGIC_VECTOR (8-1 downto 0);      -- cathodes for 7-segment
display
        jc : out STD_LOGIC_VECTOR (8-1 downto 0);      -- anodes for alarm, door,
locker
        led0_b : out STD_LOGIC;                        -- led rgb
        led0_g : out STD_LOGIC;
        led0_r : out STD_LOGIC

    );
end top;

```

Architektura TOP modulu

```

architecture Behavioral of top is
    -- No internal signals

    signal s_number : std_logic_vector(4 - 1 downto 0);

    signal s_data0 : std_logic_vector(4 - 1 downto 0);
    signal s_data1 : std_logic_vector(4 - 1 downto 0);
    signal s_data2 : std_logic_vector(4 - 1 downto 0);
    signal s_data3 : std_logic_vector(4 - 1 downto 0);

begin

    -----
    -- Instance (copy) of driver_7seg_4digits entity

```

```
uut_keypad_4x3 : entity work.keypad_4x3
  port map(
    clk      => CLK100MHZ,
    hor_1    => ja(0),
    hor_2    => ja(1),
    hor_3    => ja(2),
    hor_4    => ja(3),
    ver_1    => ja(4),
    ver_2    => ja(5),
    ver_3    => ja(6),
    number_o => s_number
  );

uut_controller : entity work.controller
  port map(
    clk      => CLK100MHZ,
    reset    => btn(0),
    number_i => s_number,
    door_i   => ja(7),
    alarm_o  => jc(7),
    locker_o => jc(6),
    data0_o  => s_data0,
    data1_o  => s_data1,
    data2_o  => s_data2,
    data3_o  => s_data3
  );

driver_seg_4 : entity work.driver_7seg_4digits
  port map(
    clk      => CLK100MHZ,
    reset    => btn(0),

    data0_i => s_data0,
    data1_i => s_data1,
    data2_i => s_data2,
    data3_i => s_data3,

    seg_o(6) => jb(6),
    seg_o(5) => jb(5),
    seg_o(4) => jb(4),
    seg_o(3) => jb(3),
    seg_o(2) => jb(2),
    seg_o(1) => jb(1),
    seg_o(0) => jb(0)
  );

end architecture Behavioral;
```

Diskuse o výsledcích

Zadání projektu jsme rozšířili o LED RGB diodu, která mění barvu podle aktuálního stavu v process controller a o alarm, který může být realizovaný sirénou. Výsledky projektu se shodují s naší představou a očekáváním. Program by bylo vhodné otestovat na hardwaru a ověřit funkčnost.

Video

https://vutbr-my.sharepoint.com/_g/personal/xhonky00_vutbr_cz/ESstso6UwhyFKhILq08kfJZEBm5fL0fUlk9VYA59FjubmrA?e=ymaxjz

Reference

<https://github.com/shahjui2000/Push-Button-Door-VHDL->

https://www.kth.se/social/files/5458faeef276544021bdf437/codelockVHDL_eng.pdf

<https://www.fpga4student.com/2017/09/vhdl-code-for-seven-segment-display.html>